

End Semester Examination

Subject: Network Theory

Class: SY B.Tech

Max. Marks: 50

Marking Scheme

- Q.1 Any five questions are to be considered .
- a. Write the incidence matrix and express branch voltages in terms of node voltages. 2 marks
 - b. The fundamental cutset matrix . Express branch voltages in terms of twig voltages. 2 marks
 - c. The fundamental cutset matrix. Draw the oriented graph. 2 marks
 - d. Draw the oriented graph. 2 marks
 - e. Explain tieset. 2 marks
 - f. Formula and explanation of possible trees of a graph. 2 marks
 - g. Draw oriented graph. 2 marks
 - h. Write tieset matrix. 2 marks
- Q. 2 a. Thevenin's Voltage and resistance $V_{TH} = 93.5V, R_{TH} = 22.75\Omega$ 2 marks
Current Through 24 ohm resistor $I_{24\Omega} = 2A$ 2 marks
- b. Norton's equivalent resistance $R_N = 0.95\Omega$ 2 marks
Current Through 10 ohm resistor $I_{10\Omega} = 0.43A$ 2 marks
- Q. 3. a. Write a short note on series resonant circuits and bandwidth 2marks
parallel resonant circuits and bandwidth. 2marks
- b. Classification 1 mark
Definition of types of filters. 3 marks
- Q. 4 a. Open-circuit impedance parameters. $Z_{11} = \frac{23}{8}, Z_{12} = Z_{21} = \frac{19}{8}, Z_{22} = \frac{31}{8}$ 2 marks
Symmetry and reciprocity. Reciprocal N/w. 2 marks
- b. Value of load impedance $Z_L = 2.64 - j0.72\Omega$ 2 marks
Find maximum power. $P_{max} = 197.07 \text{ watts}$ 2 marks
- Q.5 a. Find Y-parameters. $Y_{11} = 1/4, Y_{12} = -7/4, Y_{21} = -1/4, Y_{22} = \frac{5}{4}$ 4 marks
- b. What are ABCD parameters 2 marks
Condition for symmetry and reciprocity $A = D$ & $AD - BC = 1$ 2 marks
- Q. 6 a. T-type attenuator with diagram 2 marks
 π -type attenuator with diagram 2 marks
- b. Full series equalizer 2 marks
Full shunt equalizer. 2 marks