

Maharashtra Institute of Technology, Aurangabad

(An Autonomous Institute)

END SEMESTER EXAMINATION

Second Year B.Tech (EE) – Feb/Mar-2023

Course Code : EED201

Course Name : Electrical Machines 1

Duration : 2 Hrs

Max. Marks : 50

Date :06 Feb,2023

Instructions :

- i) All questions are compulsory
- ii) Assume suitable data wherever necessary and clearly state it
- iii) Figures to right indicate full marks

Q. 1	Answer any five (Marks:10)	Marks	CO	BL	PI
a)	Draw Characteristics of DC Shunt Motors.	2	1,2	1	1.2.1
b)	What are different losses in transformer.	2	1,2	1	2.2.3
c)	Write any 4 applications of Synchro's	2	4	1	1.2.1
d)	Draw transformer equivalent circuit referred to secondary	2	1	1	1.1.1
e)	Define Back pitch and front pitch	2	1,2	2	1.3.1
f)	Write causes of bad commutation	2	5	2	1.2.1
g)	Brief polarity test in transformer	2	1	1	1.1.1
h)	Write significance of back emf in DC motor.	2	4	2	1.1.1
Q.2	Solve both the following				
	a) An 8-pole DC shunt generator with 778 wave-connected armature conductors and running at 500 r.p.m. supplies a load of 12.5Ω resistance at terminal voltage of 50 V. The armature resistance is 0.24Ω and the field resistance is 250Ω . Find the armature current, the induced EMF and the flux per pole.	4	4	4	3.2.1
	b) Describe phasor diagram of transformer when leakage reactance is considered for capacitive load	4	4	4	3.3.2
Q.3	Solve any one from the following Describe 3 Point starter in detail with its diagram. OR A single phase transformer has 1000 turns on primary and 200 turns on secondary. The no load current is 3amp at a power factor of 0.2 lagging. Calculate the primary current and power factor when the secondary current is 280Amp at a power factor of 0.8 lagging.	8	2,3 1,2,3	3 2	2.3.2 2.3.3
Q.4	Solve both the following				
	a) Derive condition of maximum efficiency of transformer	4	1,2,3	1	1.3.2
	b) Brief low inertia DC motor in detail	4	1,2	1	
Q.5	Solve both the following				
	a) Brief about Permanent magnet DC Motor	4	4,5	3	3.3.2

	b) Discuss Delta Delta connection in 3 phase transformer	4	5	2	2.3.1
Q.6	Solve any one from the following	8	4,5,6	4	2.3.1
	a) Explain construction of DC Machine with all parts				
	OR		5	4	3.2.2
	b) Brief speed control techniques in DC Shunt motor				